$current \ gain \ = \ 57.14285714$ 

input impedance = 115485.7143ohm

voltage gain = 0.989609104

output resistance = 32558.13953ohm