

ABC

- 0. 1. 0.
- 0. 0. 0.
- 1. 1. 1.
- 0. 1. 1.
- 1. 0. 0.

The following data lines are to be given '' 1'' and remaining should be given'' $\mathbf{0}$

0.

For a 4–1 mux, we should give D0=C", D1 = "1", D2 = C' and D3 = C with A and B as data selector inputs